

Full Marks: 20

Time: 1 hour

Instruction: Write your name clearly in your answer sheet. Section 1 contains MCQ and filling in the blank and section 2 contains theoretical questions. Please write the MCQ/Filling answers in your main answer sheet indicating the question number and your choice of answer clearly. You are **not** required to copy the question (just indicate the question number clearly) in your answer sheet. You may use the last page of your main answer sheet for rough calculations.

Best of luck.

Section 1 (each question is of 1 mark)

[5 X 1 = 5marks]

1. The total resistance seen across terminal ab in Figure 1 is _____.

[a] 0.5 Ω

[b] 2 Ω

[c] 2.5 Ω

[d] 5 Ω

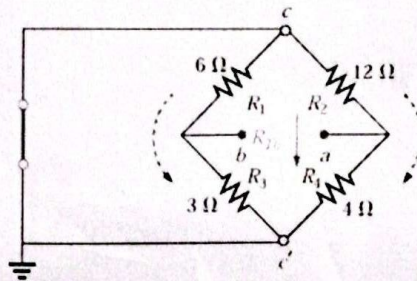


Figure: 1

2. The voltage E_{Th} in the circuit of Figure 2 is 4 V.

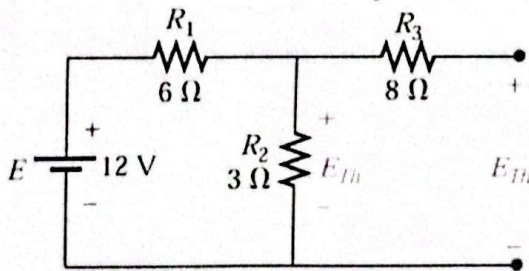


Figure 2

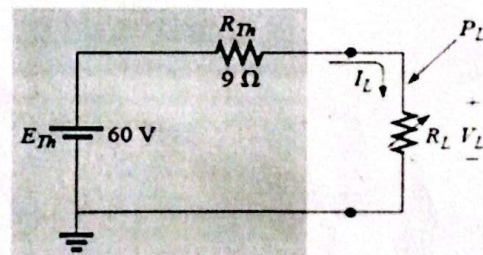


Figure 3

3. For the network in Figure 3, power delivered to the load (P_L) is given by _____.

[a] $\frac{3600}{4R_L}$

[b] $\frac{3600}{16R_L}$

[c] $\frac{3600R_L}{(9\Omega + R_L)^2}$

[d] $\frac{3600R_L}{16(9\Omega + R_L)^2}$

4. The current in open circuit is _____.

[a] minimum

[b] maximum

[c] negative

[d] zero

5. For a star delta network with equal resistance, in general, _____.

[a] $R_Y = R_\Delta/3$



[b] $R_Y = 3R_\Delta$

[c] $R_Y = R_\Delta/\sqrt{3}$

[d] $R_Y = \sqrt{3}R_\Delta$


Section 2

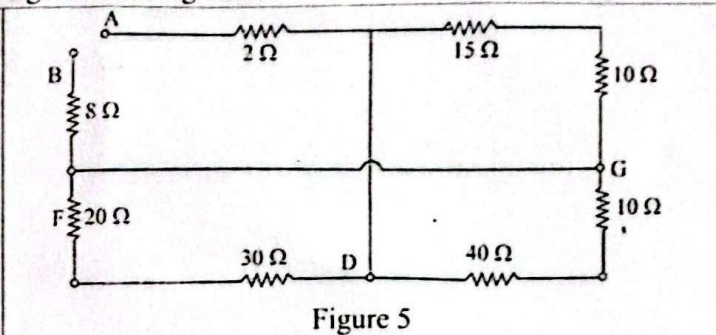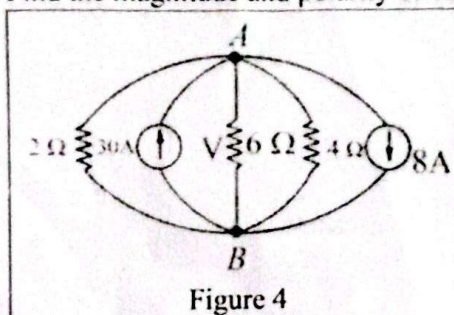6. Find the magnitude and polarity of voltage V in the figure 4. [3 marks]



→ 22.5 ohm

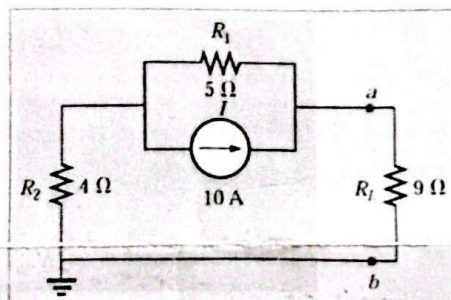7. In figure 5 shown above, find the equivalent resistance R_{AB} across points A and B. [4 marks]
8. Find the Norton equivalent circuit for the network external to the 9-ohm resistor. [4 marks]



9. Using superposition, find the current through the R_1 resistor for the networks of figure-7. [4 marks]

